

1 Problem 1

1.1 $Y = AC + \overline{A}\overline{B}C$

$$Y = AC + \overline{A}\overline{B}C$$

$$Y = C(A + \overline{A}\overline{B})$$

$$Y = C(A + \overline{A}\overline{B})$$

Truth Table:

A	B	C	AC	$\overline{A}\overline{B}C$	Y
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	0	1

K-Map:

	AB				
C		00	01	11	10
	0	0	0	0	0
	1	1	0	1	1

1.2 $Y = \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{(A + C)}$

$$Y = \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{(A + C)}$$

$$Y = \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{A}C$$

$$Y = \overline{A}(\overline{B} + B\overline{C} + C)$$

$$Y = \overline{A}(\overline{B} + \overline{\overline{B}\overline{C}} + C)$$

$$Y = \overline{A}(\overline{B} + \overline{\overline{B} + C} + C)$$

$$Y = \overline{A}((\overline{B} + C) + (\overline{\overline{B} + C}))$$

$$Y = \overline{A}$$

Truth Table:

A	B	C	$\overline{A}\overline{B}$	$\overline{A}B\overline{C}$	$\overline{(A+C)}$	Y
0	0	0	1	0	0	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	1	0	0	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	0

K-Map:

		AB			
C		00	01	11	10
	0	1	1	0	0
	1	1	1	0	0

2 Problem 2

2.1 Part 1

A	B	C	Y	Minterm
0	0	0	1	$\overline{A}\overline{B}\overline{C}$
0	0	1	0	-
0	1	0	0	-
0	1	1	0	-
1	0	0	0	-
1	0	1	0	-
1	1	0	0	-
1	1	1	1	ABC

$$Y = \overline{A}\overline{B}\overline{C} + ABC$$

2.2 Part 2

A	B	C	Y	Minterm
0	0	0	1	$\overline{A}\overline{B}\overline{C}$
0	0	1	0	-
0	1	0	1	$\overline{A}B\overline{C}$
0	1	1	0	-
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	-
1	1	0	1	$AB\overline{C}$
1	1	1	0	-

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + AB\overline{C}$$

3 Problem 3

3.1 Part 1

Already minimal

3.1.1 Part 2

K-Map:

	AB				
C		00	01	11	10
	0	1	1	1	1
	1	0	0	0	0

$$Y = \overline{C}$$

4 Problem 4

f is true except when x_1 , $\overline{x_2}$ and x_3 are all true (term 5), i.e. it is the negation of $x_1\overline{x_2}x_3$:

$$\begin{aligned} f(x_1, x_2, x_3) &= \overline{x_1\overline{x_2}x_3} \\ f(x_1, x_2, x_3) &= \overline{x_1} + x_2 + \overline{x_3} \end{aligned}$$

K-Map:

	x_1x_2				
x_3		00	01	11	10
	0	1	1	1	1
	1	1	1	1	0

$$f(x_1, x_2, x_3) = \overline{x_1} + x_2 + \overline{x_3}$$

5 Problem 5

5.1 Part 1

Sum of Products:

x_1	x_2	x_3	$f(x_1, x_2, x_3)$	Minterm
0	0	0	0	-
0	0	1	1	$\overline{x_1}\overline{x_2}x_3$
0	1	0	0	-
0	1	1	0	-
1	0	0	1	$x_1\overline{x_2}\overline{x_3}$
1	0	1	1	$x_1\overline{x_2}x_3$
1	1	0	1	$x_1x_2\overline{x_3}$
1	1	1	0	-

$$Y = \overline{x_1} \overline{x_2} x_3 + x_1 \overline{x_2} \overline{x_3} + x_1 \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$$

K-Map:

		$x_1 x_2$			
		00	01	11	10
x_3	0	0	0	1	1
	1	1	0	0	1

$$Y = x_1 \overline{x_2} + x_1 \overline{x_3} + \overline{x_2} x_3$$

Minimize:

$$Y = \overline{x_1} \overline{x_2} x_3 + x_1 \overline{x_2} \overline{x_3} + x_1 \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$$

$$Y = \overline{x_1} \overline{x_2} x_3 + x_1 \overline{x_2} (\overline{x_3} + x_3) + x_1 x_2 \overline{x_3}$$

$$Y = \overline{x_1} \overline{x_2} x_3 + x_1 \overline{x_2} + x_1 x_2 \overline{x_3}$$

$$Y = x_1 \overline{x_2} + \overline{x_1} \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$$

$$Y = x_1 \overline{x_2} + \overline{x_1} \overline{x_2} x_3 + x_1 x_2 \overline{x_3}$$

Product of sums:

x_1	x_2	x_3	$f(x_1, x_2, x_3)$	Maxterms
0	0	0	0	$x_1 + x_2 + x_3$
0	0	1	1	-
0	1	0	0	$x_1 + \overline{x_2} + x_3$
0	1	1	0	$x_1 + \overline{x_2} + \overline{x_3}$
1	0	0	1	-
1	0	1	1	-
1	1	0	1	-
1	1	1	0	$\overline{x_1} + \overline{x_2} + \overline{x_3}$

$$Y = (x_1 + x_2 + x_3)(x_1 + \overline{x_2} + x_3)(x_1 + \overline{x_2} + \overline{x_3})(\overline{x_1} + \overline{x_2} + \overline{x_3})$$

5.2 Part 2

Sum of Products:

x_1	x_2	x_3	$f(x_1, x_2, x_3)$	Minterm
0	0	0	1	$\overline{x_1} \overline{x_2} \overline{x_3}$
0	0	1	x	-
0	1	0	1	$\overline{x_1} x_2 x_3$
0	1	1	1	$\overline{x_1} x_2 x_3$
1	0	0	1	$x_1 \overline{x_2} \overline{x_3}$
1	0	1	x	-
1	1	0	0	-
1	1	1	0	-

$$Y = \overline{x_1} \overline{x_2} \overline{x_3} + \overline{x_1} x_2 x_3 + \overline{x_1} x_2 x_3 + x_1 \overline{x_2} \overline{x_3}$$

K-Map:

	x_1x_2				
x_3		00	01	11	10
	0	1	1	0	1
	1	x	1	0	x

$$Y = \overline{x_1} + \overline{x_2}$$

6 Problem 6

Truth Table:

A	B	C	D	Y
0	0	0	0	x
0	0	0	1	x
0	0	1	0	x
0	0	1	1	0
0	1	0	0	0
0	1	0	1	x
0	1	1	0	0
0	1	1	1	x
1	0	0	0	1
1	0	0	1	0
1	0	1	0	x
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	x
1	1	1	1	1

K-Map:

	AB				
CD		00	01	11	10
	00	x	0	1	1
	01	x	x	1	0
	11	0	x	1	1
	10	x	0	x	x


Minimal:

$$Y = AB + AC + BD$$

Problem 7

Problem 7

Circuit

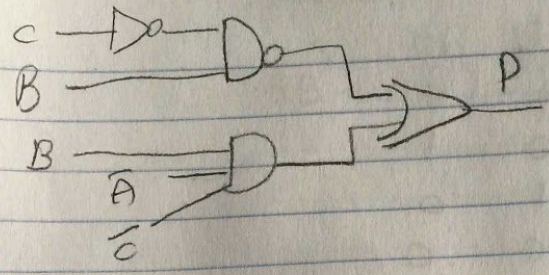

Minimal-cost expression


$$P = \bar{A}B\bar{C} + (\bar{B}\bar{C}) = \bar{A}B\bar{C} + \bar{B} + C$$

$$= \bar{A}\cancel{B} + C + \bar{B} = \bar{A} + \bar{B} + C$$

Truth table

A	B	C	P
0	0	0	1
0	0	1	1
0	1	0	1 ✓
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

K-map

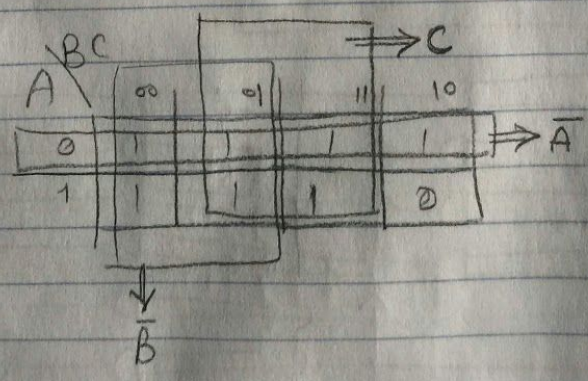

Problem 8

problem 8

2-to-4 decoder truth table

i_1	i_0	d_3	d_2	d_1	d_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

3-to-8 decoder truth table

i_2	i_1	i_0	d_7	d_6	d_5	d_4	d_3	d_2	d_1	d_0
-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------


0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

Circuit of 3-to-8 decoder

Cost of n-to- 2^n decoder

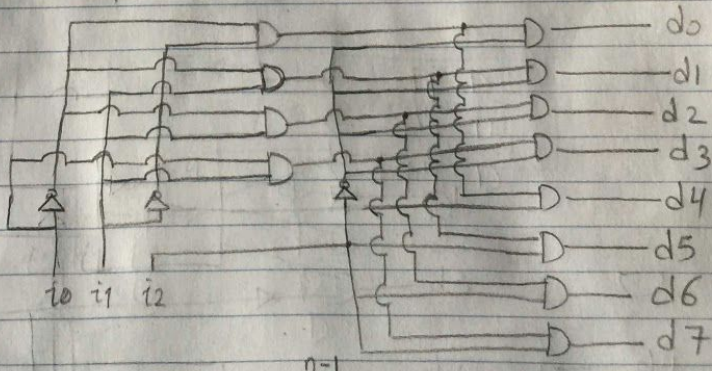

2-input AND gates = 3×2
 # NOT gates = n


Problems 9 and 10

Problem 9


$$Y = \bar{A}\bar{B} + (\bar{A}B + A\bar{B})\bar{C}\bar{D}$$

Problem 10


1

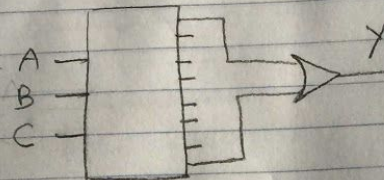


2

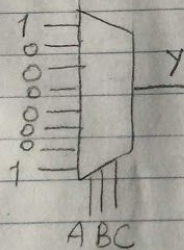

3

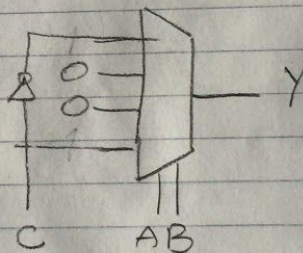


4

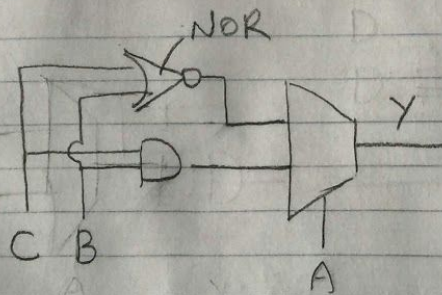

(Assuming NOR is okay)

Problem 11

$$Y = A + \bar{A}(\bar{C}\bar{D} + CD)$$

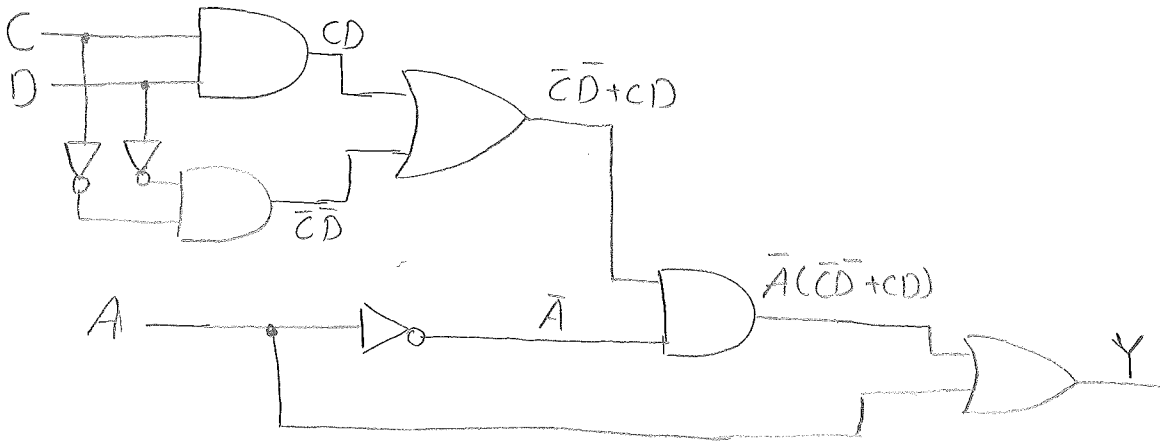


simplification: $a + \bar{a}b = a + b \Rightarrow Y = A + \bar{C}\bar{D} + CD$

or using K-map


	CD	00	01	11	10
A		0	1	1	1
		1	1	1	1

$\Rightarrow A + \bar{C}\bar{D} + CD$

Circuit:

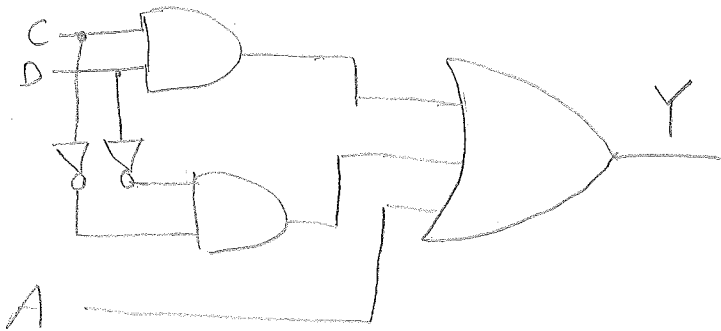


more simplification: $\bar{C}\bar{D} + CD = \overline{C \oplus D} \equiv \text{XNOR}$

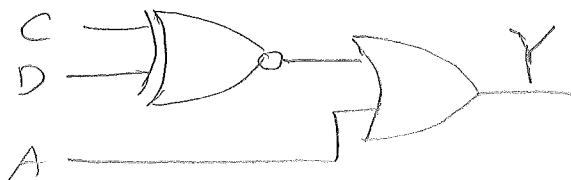


Problem 12 :

$E \equiv$ Enable of the circuit

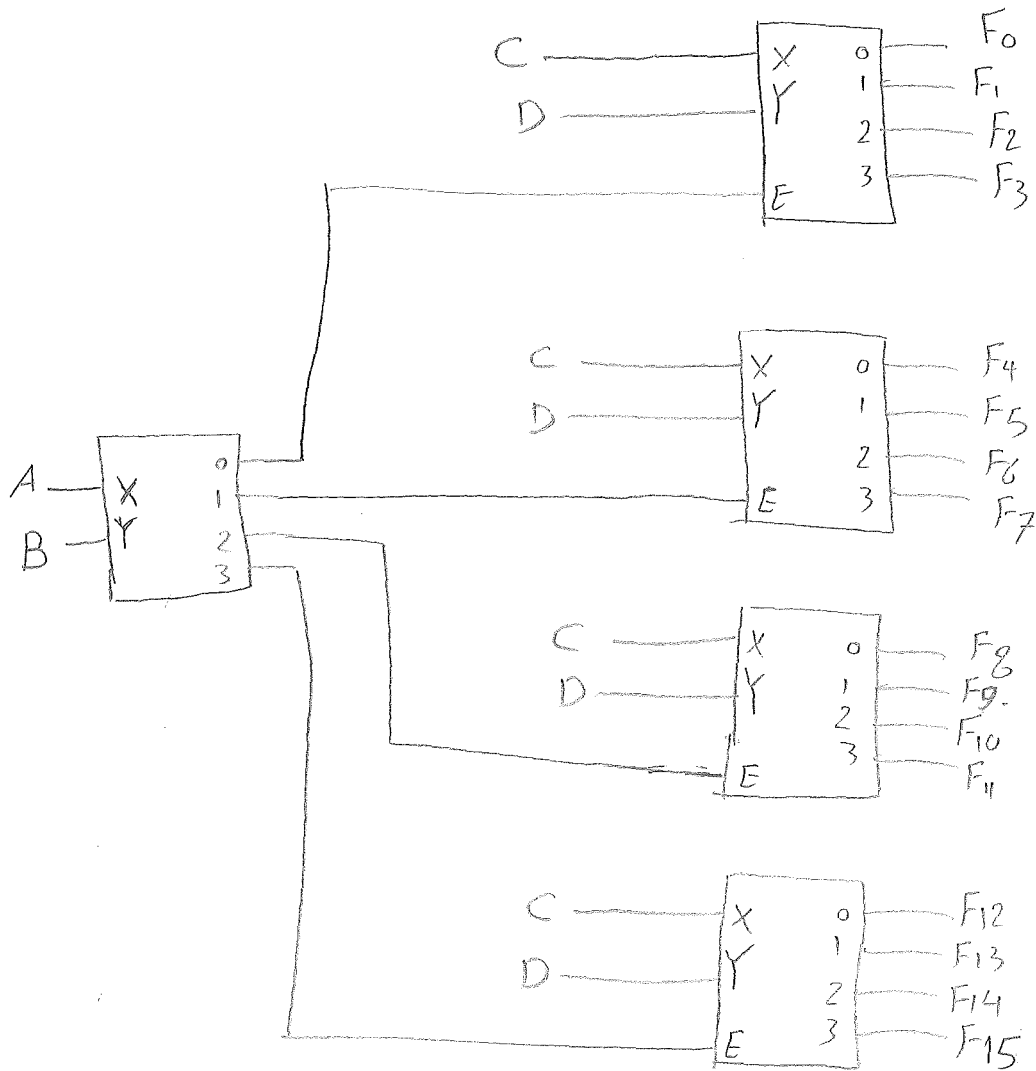


Problem 13

①

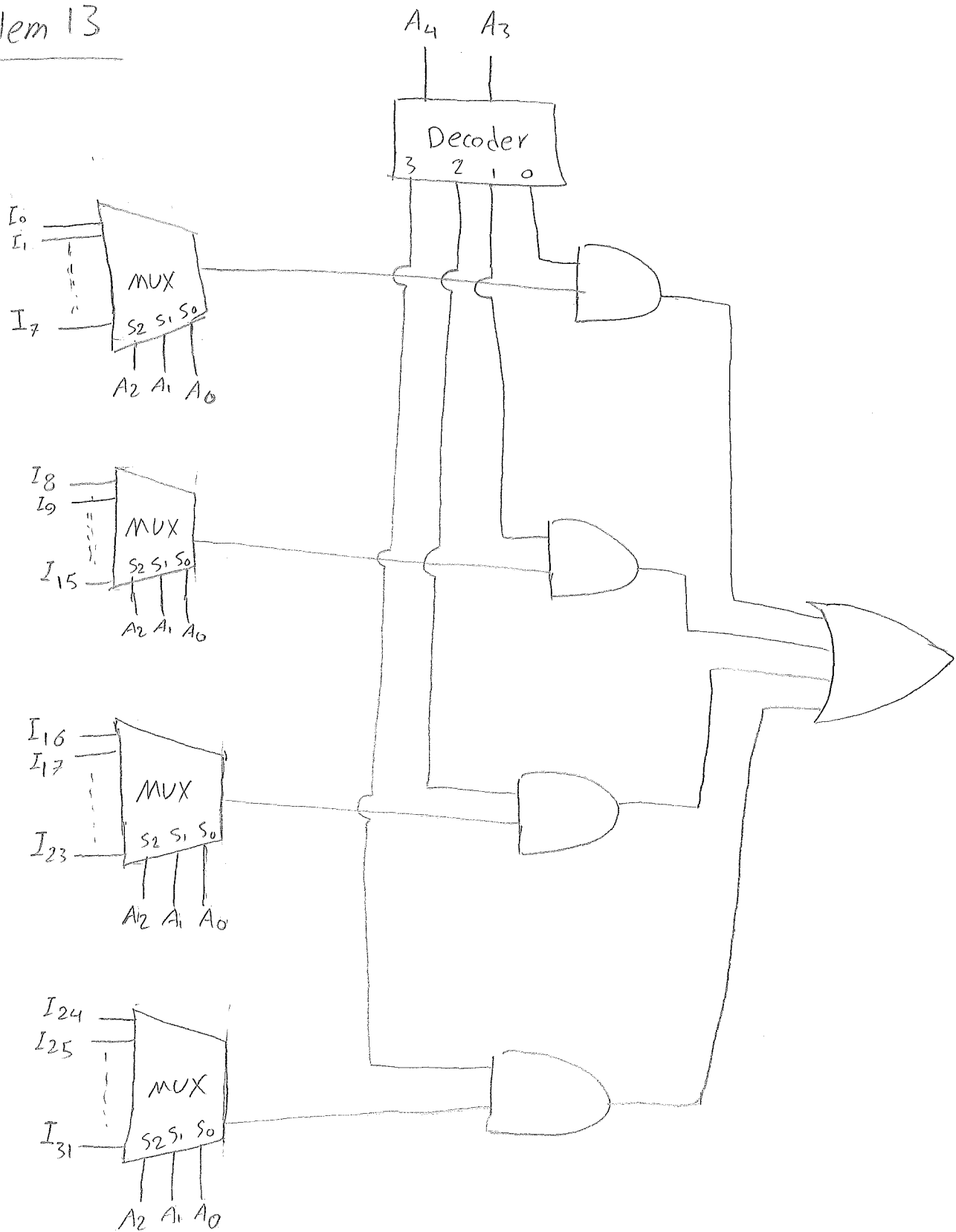


2

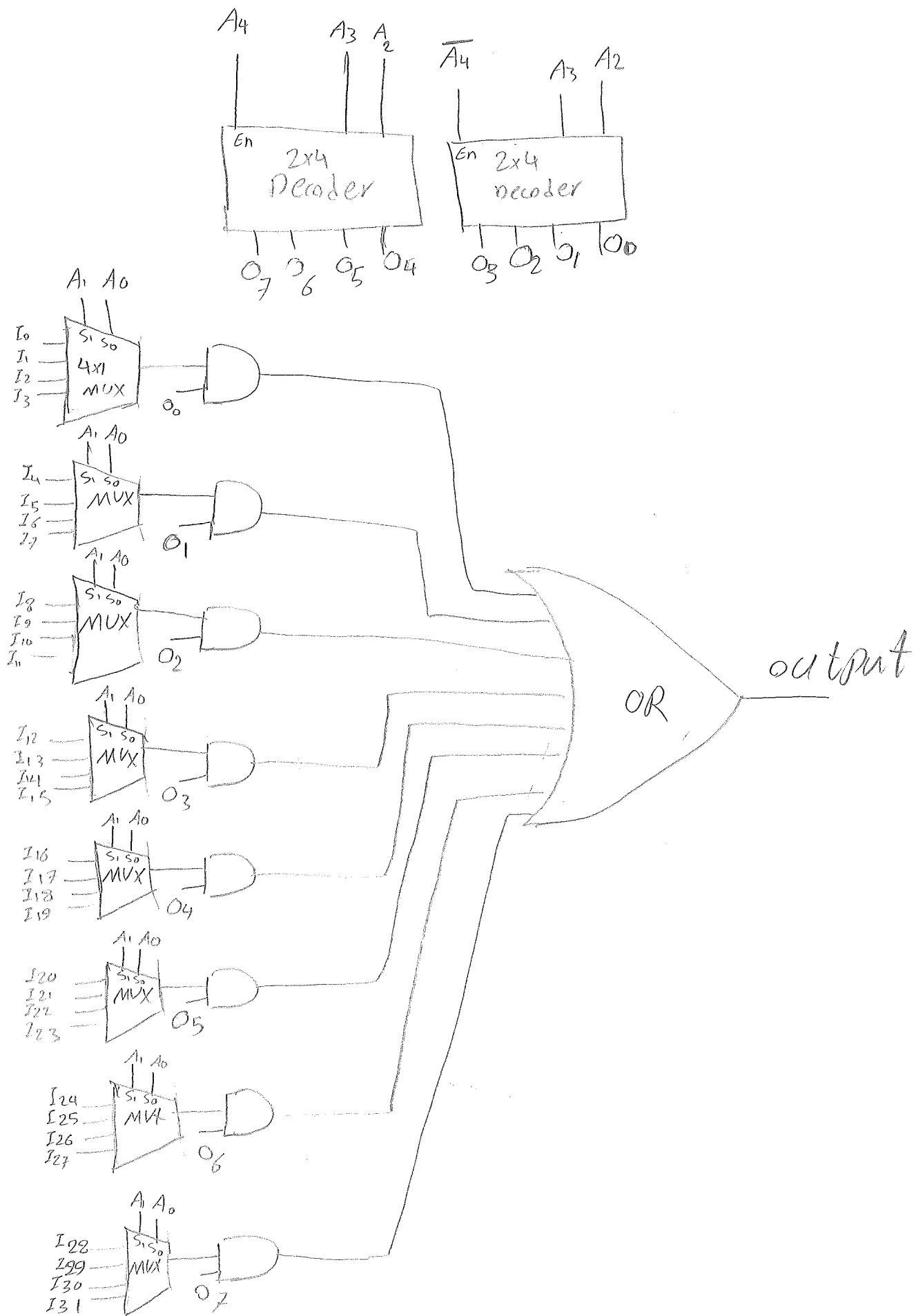


Problem 14


①

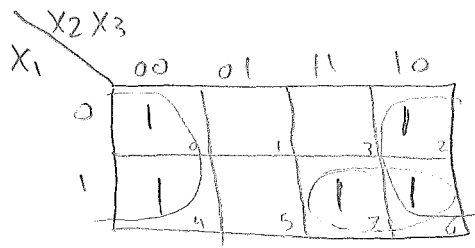


$$= \overline{X_3} + X_1 X_2$$

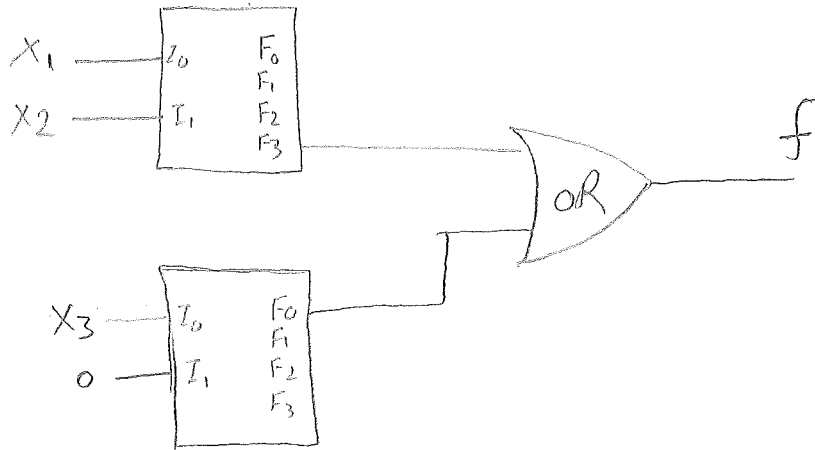

②

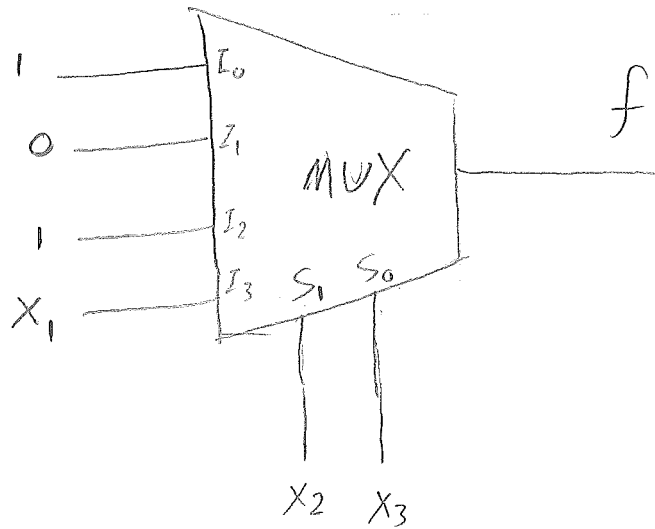

Problem 15

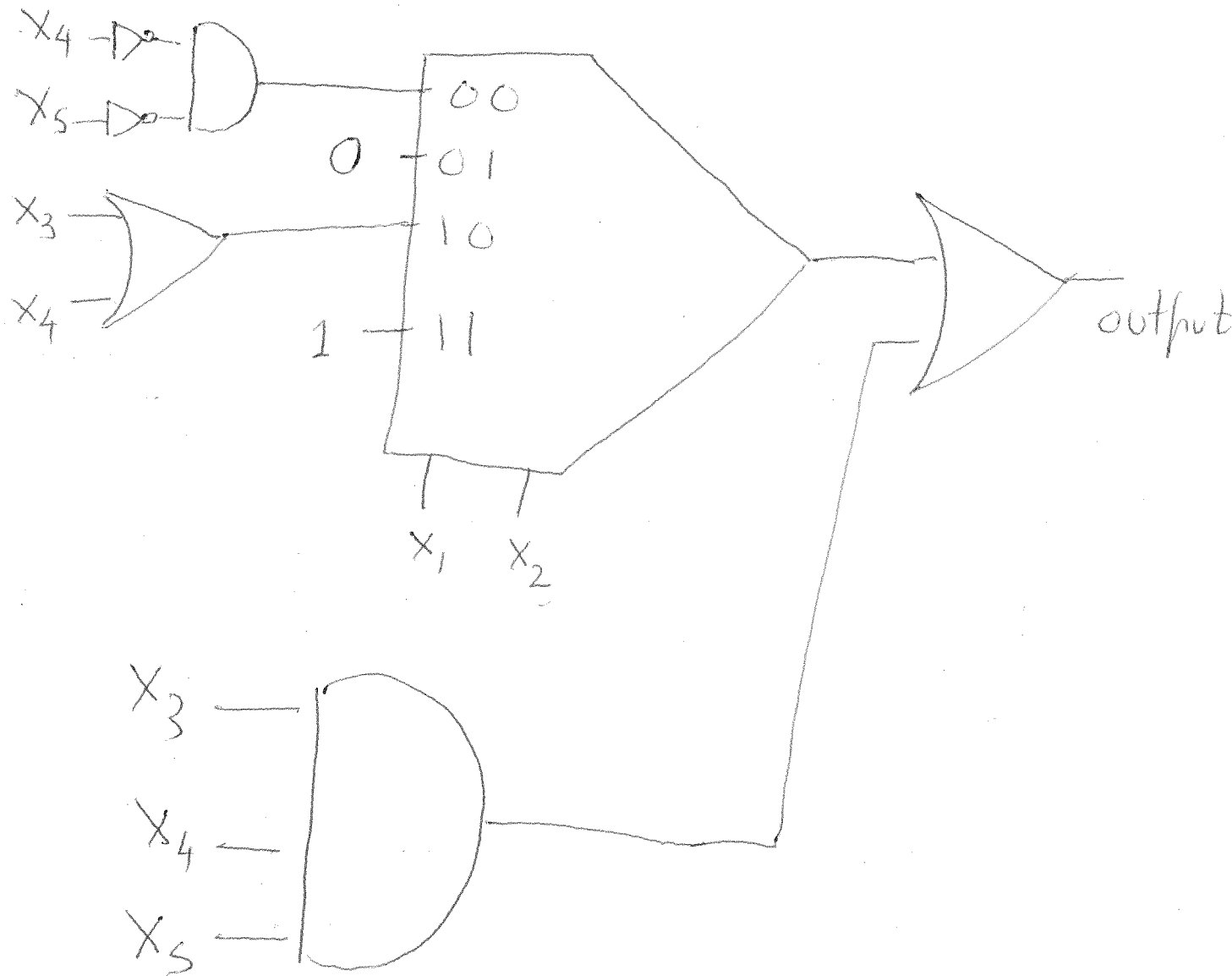


Problem 16:


①

$$f = x_1 \bar{x}_2 + \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3$$
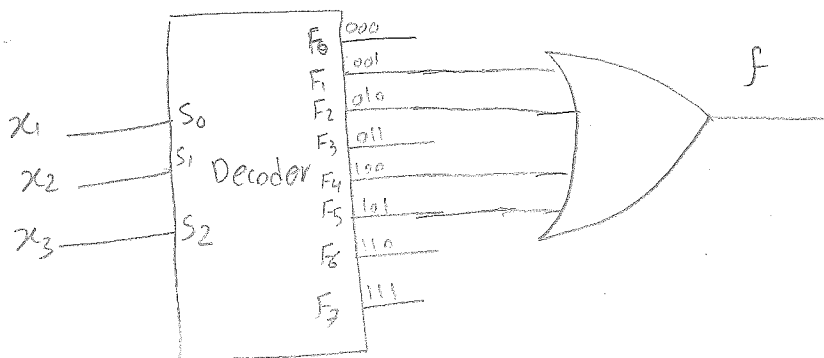
$$f = x_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 \bar{x}_2 x_3 + \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3$$



②

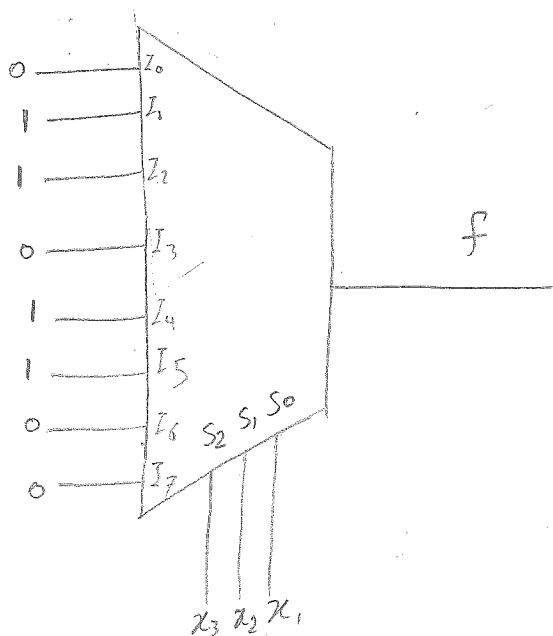

Problem 17

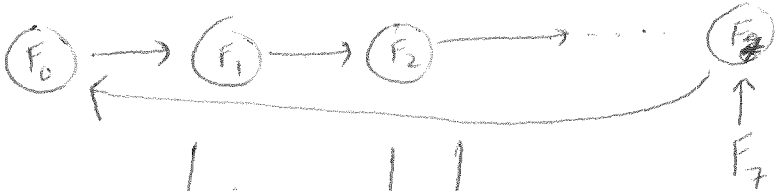
Need to maintain 3 bits. Say A B C. 8 states. F_0, \dots, F_7 where F_0 is 000 and F_8 is 100 and rest are in gray sequence.  Use ABC to maintain state.

Table:

A	B	C	A_N	B_N	C_N
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

Expression for A_N

C	AB			
	00	01	11	10
0		1	1	
1			1	1

$$A_N = B\bar{C} + AC$$

Exp for B_N

C	AB			
	00	01	11	10
0		1	1	
1	1	1		


$$B_N = B\bar{C} + \bar{A}C$$

C_N :



C	AB			
	00	01	11	10
0	1		1	
1	1		1	

$$C_N = \bar{A}\bar{B} + AB$$

Circuit:-

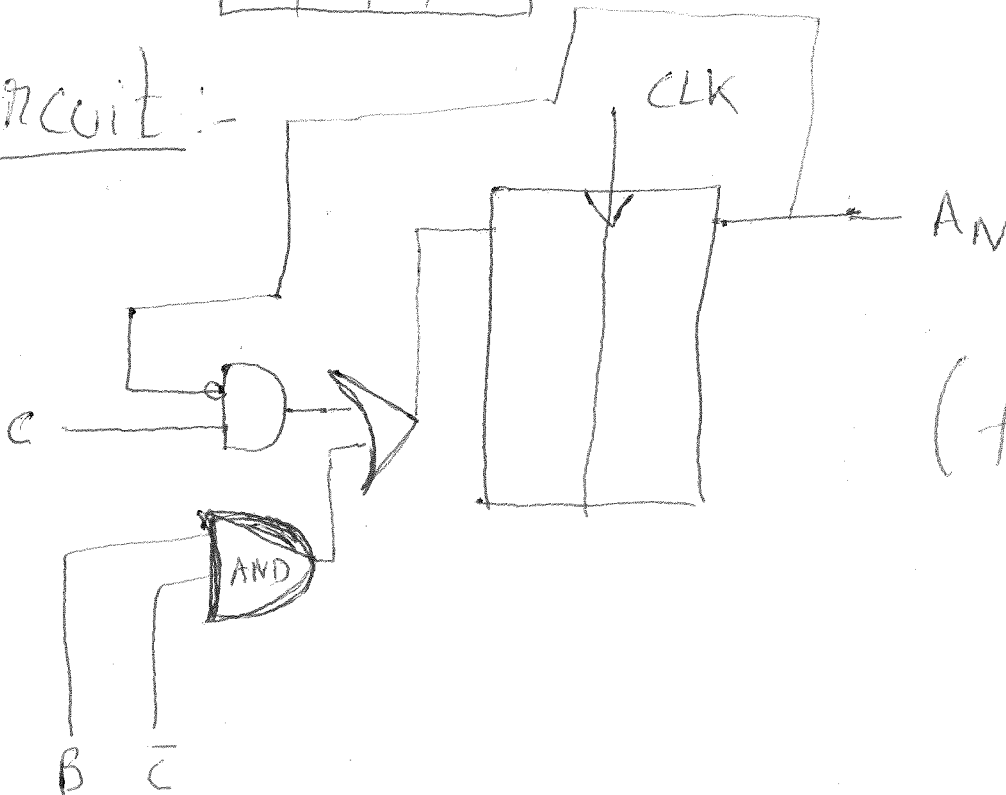


(for A_N)

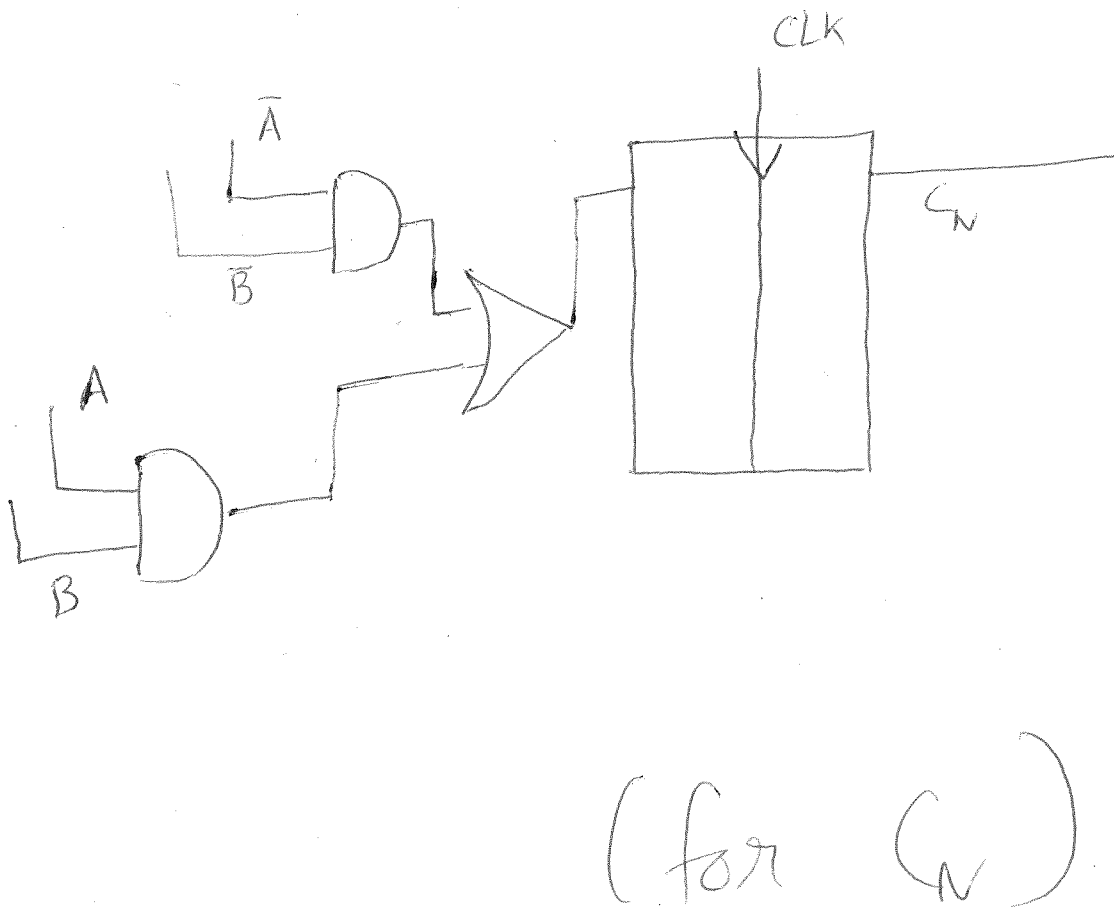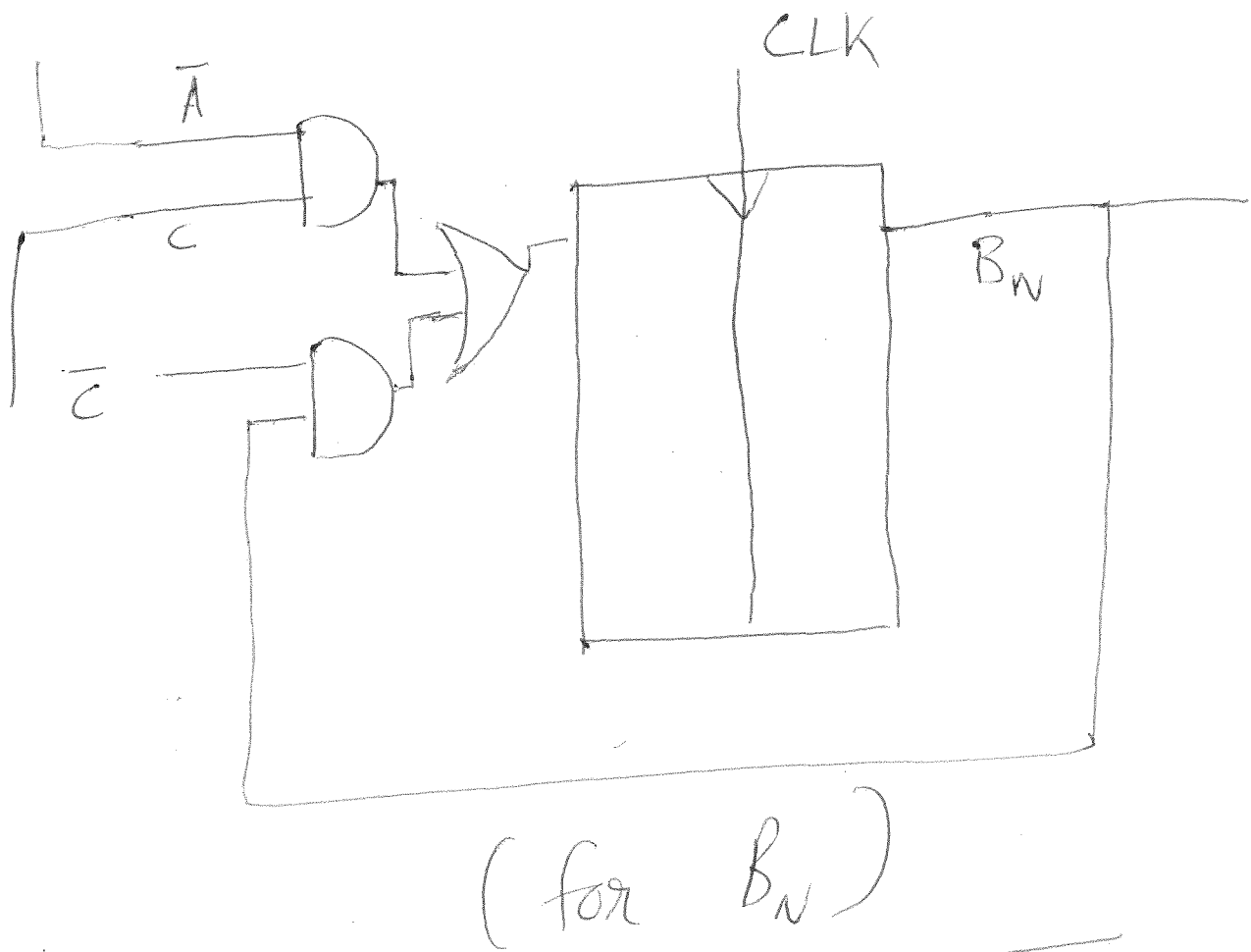

Problem 18: Let's first draw the

FSM:

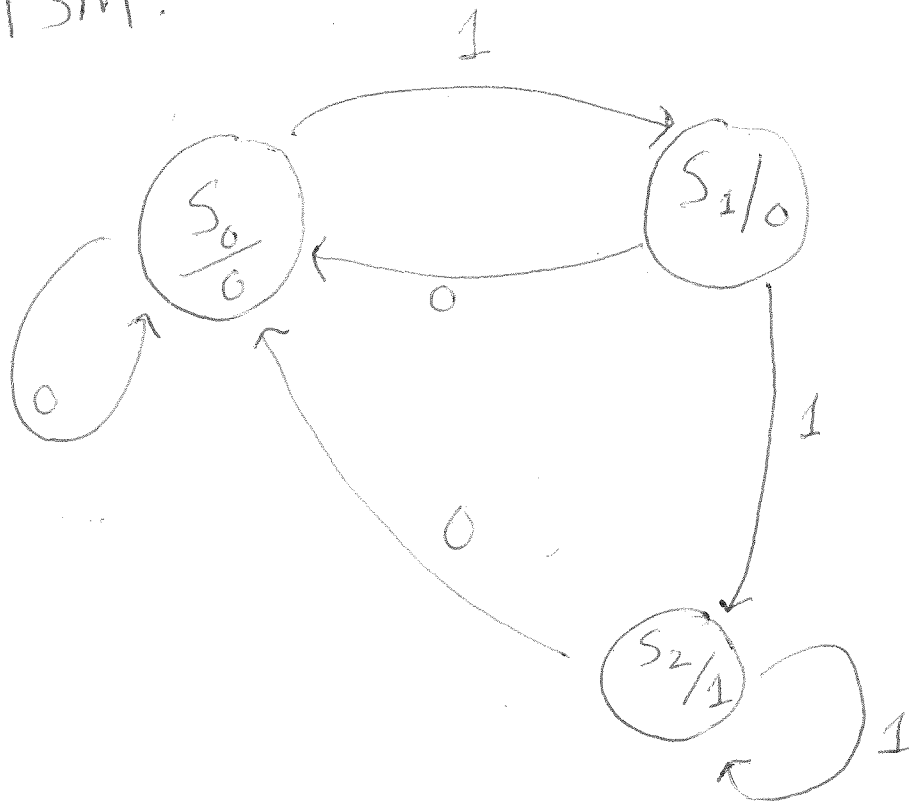

$S_0 = 00$
 $S_1 = 01$
 $S_2 = 10$

$D \equiv \text{input}$
 $Y \equiv \text{output}$

Table

A	B	D	A_N	B_N	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	1

Karnaugh maps to obtain expressions
for $A_N = f(A, B, D)$ and $B_N = g(A, B, D)$

AB \ D	00	01	11	10
0				
1		1	X	1

$$A_N = D(B + A)$$

AB \ D	00	01	11	10
0			X	
1	1		X	

$$B_N = D\bar{A}\bar{B}$$

$$Y = A_N \bar{B}_N$$

(is 1 only when)
 $A_N B_N = 10$

Circuit :-

